

Exam location: Study Party in the Woz!

**Note:** These problems were unused from previous semesters, so we are releasing them for extra practice. The distribution of concepts is NOT indicative of the distribution of concepts on the actual midterm. These problems did *not* go through as extensive a filter before being released to students. In addition, there may be references to concepts that were not taught this semester. In particular, if you come across ‘nodal analysis’ it’s just another name for ‘Analyze a circuit to find all voltages/current flows using KCL/KVL/Ohm’s Law.’


## Section 1: Straightforward questions

*Unless told otherwise, you must show work to get credit. There will be very little partial credit given in this section. Each problem is worth 8 points.*


### 1. KVL/KCL Practice

**Note:** A box represents a resistor.

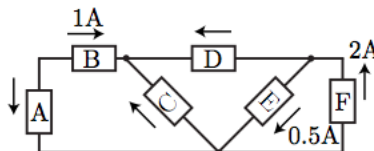
- (a) Use KCL to find the values of  $i_a$  (the current through element A),  $i_c$ , and  $i_d$  for the circuit shown below. Use the arrows as the sign convention for currents. Which elements are connected in series?



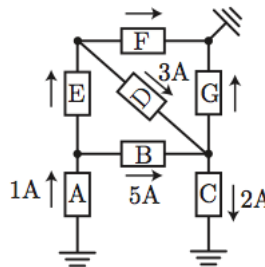
- (b) Use KCL to find the values of  $i_e$ ,  $i_f$ , and  $i_g$  for the circuit shown below. Which elements are connected in series?



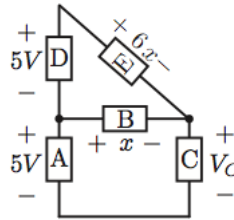- (c) In the circuit below,  $x$  denotes some unknown real number. Use KVL to find the values of  $v_b$  (the voltage difference across element  $B$ ),  $v_c$ , and  $v_e$  for the circuit shown below. Which elements are connected in shunt (i.e. parallel)?



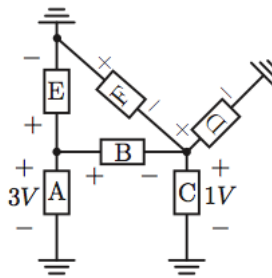
- (d) Use KVL to find the values of  $v_b$ ,  $v_d$ ,  $v_e$  and  $v_f$  for the circuit shown below. Which elements are connected in shunt?




## 2. More KCL/KVL Analysis

Using techniques presented in class, label all unknown voltages (for every node/junction) and apply KCL to find them all (with respect to ground).

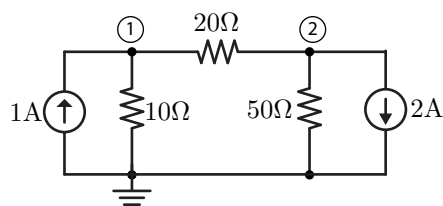
- (a) Solve for all node voltages (with respect to ground) using KCL/KVL analysis. Verify with superposition.



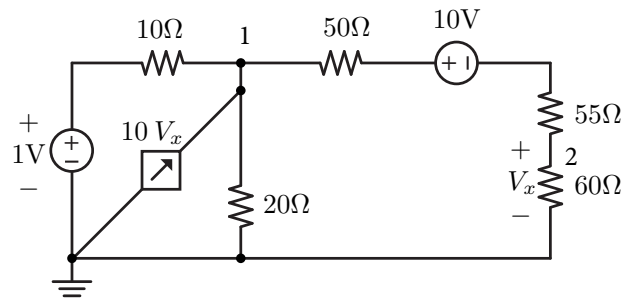- (b) Solve for all node voltages (with respect to ground) using KCL/KVL analysis.




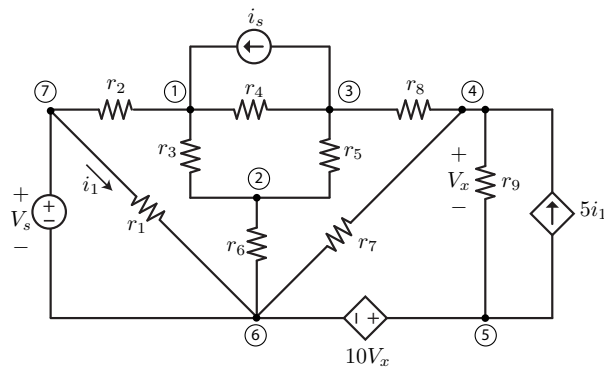- (c) Setup a matrix of equations in the form  $Av = b_s$  using KCL/KVL analysis. The vector  $v = (v_1 \ v_2 \ \dots)^T$  (use the node numbers given in the schematic).




### 3. KCL/KVL Analysis + Capacitors

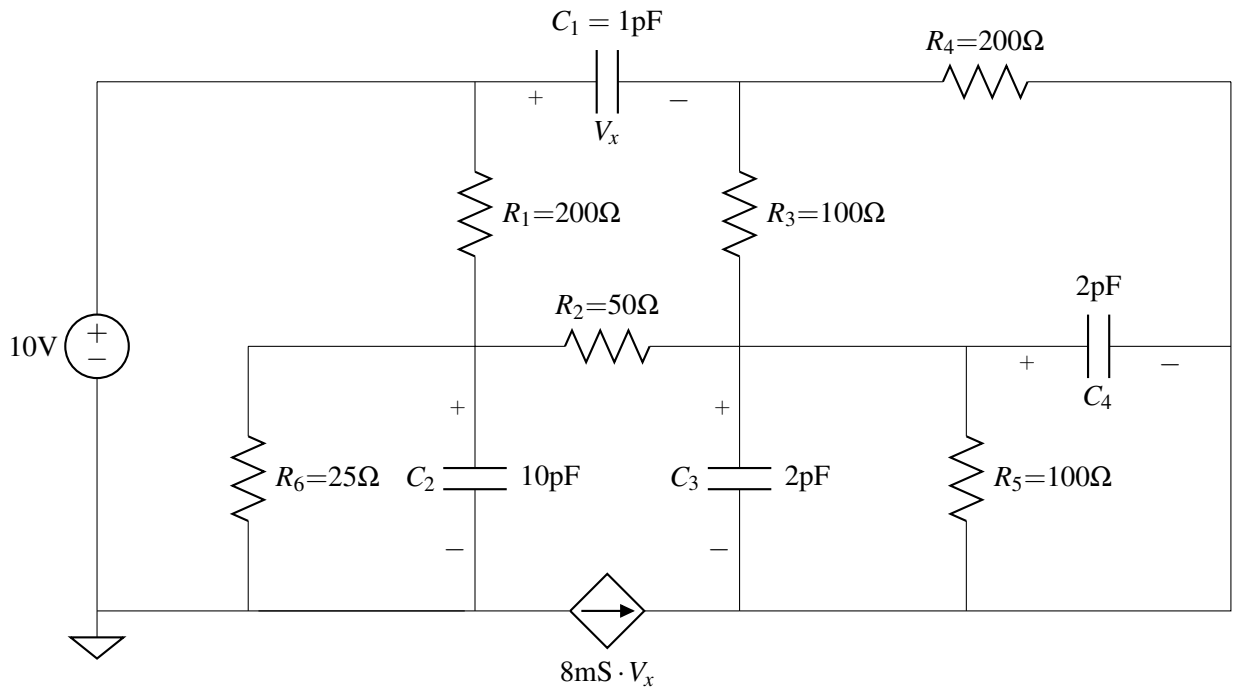- (a) Solve the following circuit in steady state using KCL/KVL analysis.




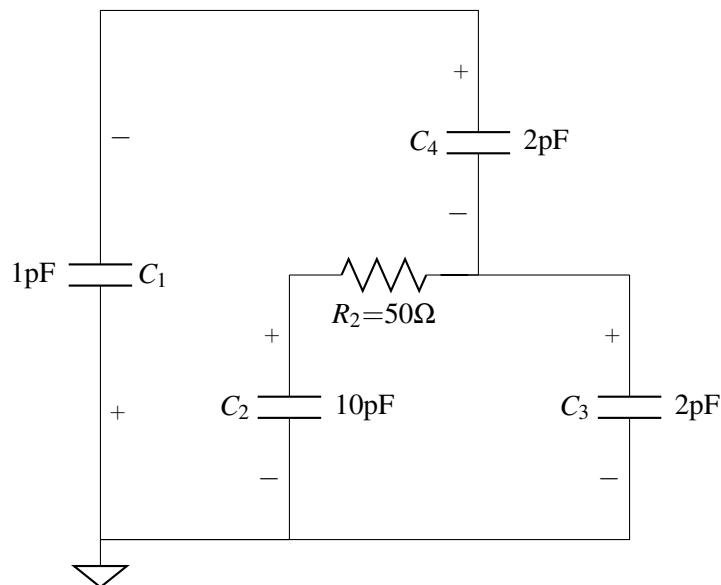- (b) After the circuit settles in steady-state from the previous part, disconnect the charged capacitors from the circuit and connect them in the configuration shown below. Polarity from part (a) is preserved. What are the voltages across, currents through and charge stored in each of the capacitors  $C_1, C_2, C_3$  and  $C_4$  in steady-state after the charge redistributes itself?




#### 4. KCL/KVL Or Superposition?

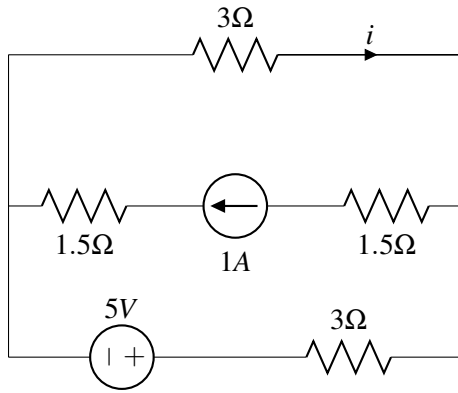- (a) Solve for the current through the  $3\Omega$  resistor, marked as  $i$ , using superposition. Verify using nodal analysis. You can use IPython to solve the system of equations if you wish. Where did you place your ground, and why?




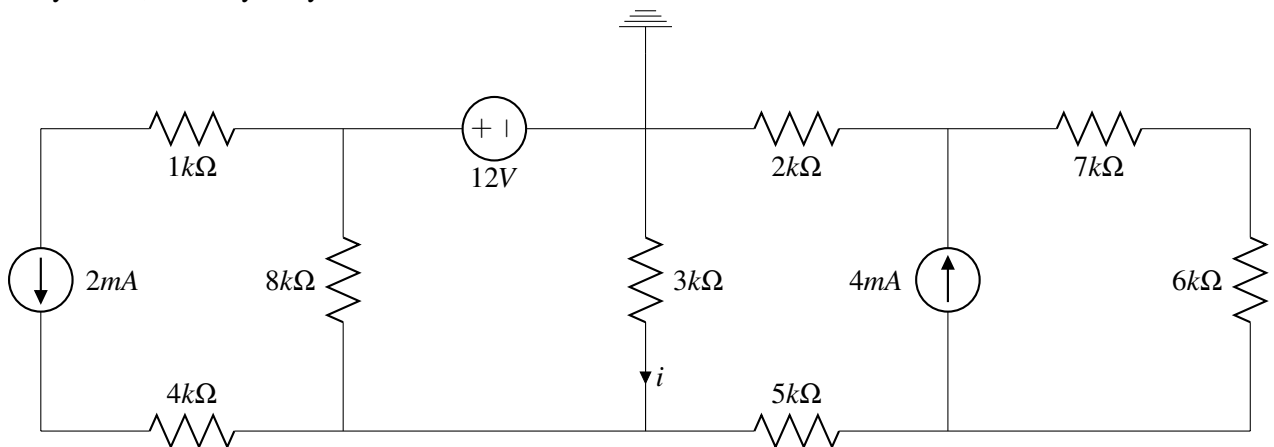- (b) Solve for the current through the  $3k\Omega$  resistor, marked as  $i$ , using whatever method you want. This problem is more mechanically tedious than the rest, so we recommend using iPython. Which method did you use, and why did you chose it?



## 5. Capacitor Charge Sharing

Consider the following circuit:

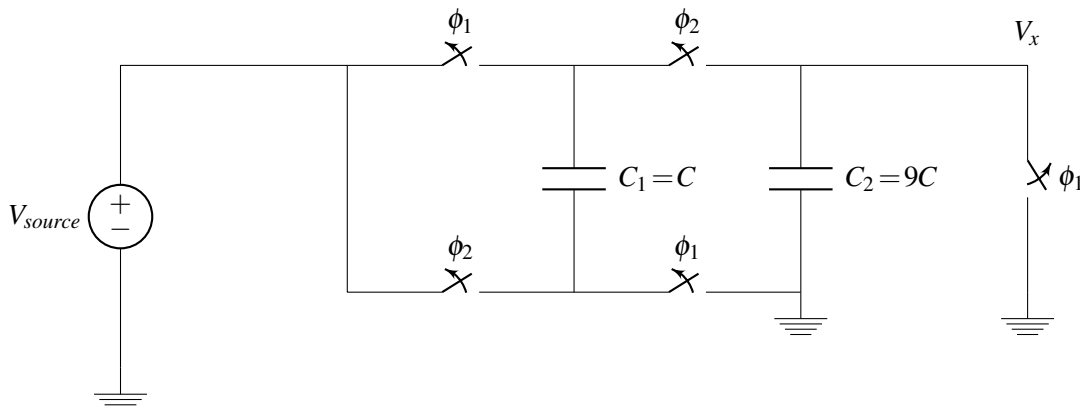


In the first phase, all of the switches labeled  $\phi_1$  will be closed and all switches labeled  $\phi_2$  will be open. In the second phase, all switches labeled  $\phi_1$  open and all switches labeled  $\phi_2$  close.

- (a) Draw polarity (+ and - signs) on the two capacitors  $C_1$  and  $C_2$ . (It doesn't matter which terminal you label + or -; just remember to keep these consistent through phases 1 and 2!)

- (b) Draw the circuit in the first phase and in the second phase. Keep your polarity in part (a) in mind.
- (c) Find the voltages and charges on  $C_1$  and  $C_2$  in the first phase. Be sure to keep the polarities of the voltages the same!
- (d) Now, in the second phase, find the voltage  $V_x$ .
- (e) (BONUS) If capacitor  $C_2$  did not exist (i.e., had a capacitance of 0F), what would the voltage  $V_x$  be?
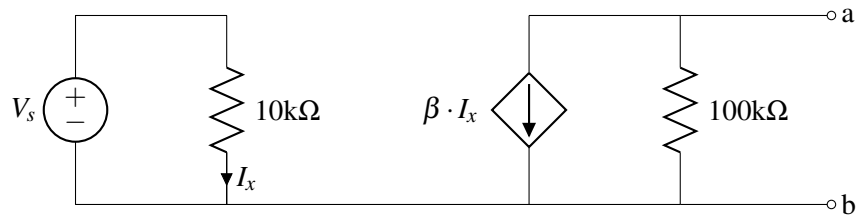
## 6. Equivalence


Find the Thévenin and Norton equivalents of the following circuit across the terminals  $a$  and  $b$  (in terms of  $V_s$  and  $\beta$ ). Note that the current source is dependent on the current  $I_x$ .




## Section 2: Free-form Problems
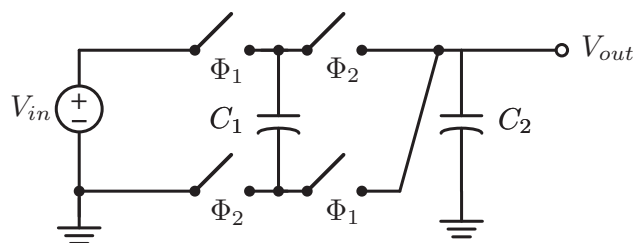
### 7. DC-DC Voltage Divider

As we have learned in class, one of the reasons for using AC voltages is that we can easily transform the voltage (step up or step down) using transformers. Unfortunately, such circuits do not work at DC and we need to come up with other ways of dividing DC voltages. We have learned about resistive dividers, but we found issues such as inefficiencies. An alternative circuit, a capacitive charge pump, is shown below. It relies on two switches which are activated in sequence, first switch  $\Phi_1$  is closed (during this period  $\Phi_2$  switches are open), and next  $\Phi_2$  closes and  $\Phi_1$  is opened. In practice this is done periodically but for this problem we will analyze each phase separately. Note that  $V_{in}$  is a DC voltage.



- During phase  $\Phi_1$ , calculate the voltage across and charge stored by each capacitor  $C_1$  and  $C_2$ .
- During phase  $\Phi_2$ , calculate the output voltage  $V_{out}$  and show that it is a fraction of the input voltage  $V_{in}$ .
- For the special case of  $C_1 = C_2$ , calculate the output voltage and the efficiency of the system. To calculate the efficiency, calculate the energy stored in the capacitors during the end of phase  $\Phi_1$  and  $\Phi_2$ .
- Assume that this circuit is used with a load represented by the current source  $I_L = 10\text{mA}$ . Suppose that the cycle described above repeats periodically at a rate of 10 kHz, or 10,000 times per second, with each phase  $\Phi_1$  and  $\Phi_2$  exactly 50% of each cycle. During phase  $\Phi_2$ , which lasts  $50\mu\text{s}$ , we wish the output voltage to not droop by more than 5mV. Specify the size of  $C_1$  and  $C_2$  to satisfy this constraint.


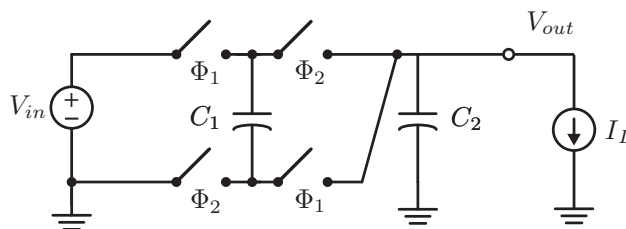


### 8. Thevenin's Theorem And Op-Amp Circuits!

You're given the below circuit – which cascades two opamps.

We're going to explore what this circuit does in several different ways.

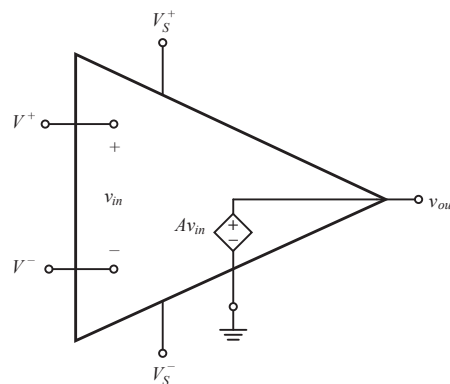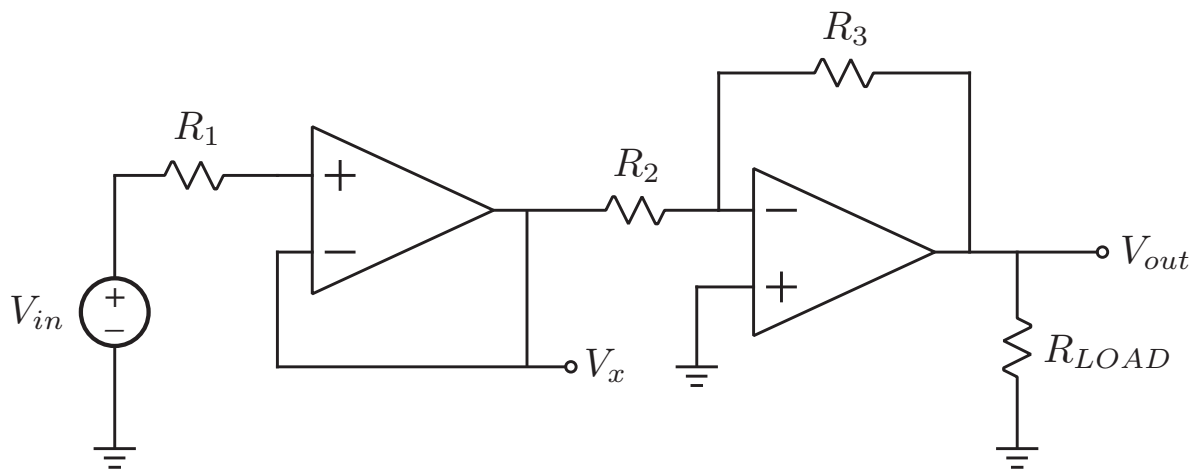- Let's first assume that the Golden Rules hold ( $A = \infty$  for both the opamps) Calculate  $V_x$  in terms of  $V_{in}$ . Calculate  $V_{out}$  in terms of  $V_x$ , and therefore in terms of  $V_{in}$ .




- (b) Now, suppose we remove the infinite gain assumption. The model of the op amp remains the same, but now  $A$  is finite for both opamps. This complicates our analysis...Thevenin and Norton, save us!  
What is the Thevenin equivalent circuit at  $V_x$  with respect to ground *looking back*? (Imagine that you disconnect the rest of the circuit to the right of node  $x$ . Look at the rest of the circuit, and find the Thevenin voltage and equivalent resistance.)
- (c) Redraw the circuit using the Thevenin equivalent you have obtained. Does it look simpler?
- (d) Now, calculate the Thevenin equivalent circuit at  $V_{out}$  with respect to ground *looking back*. (Under the same finite-gain assumption as the previous part).
- (e) Now, calculate  $V_{out}$  in the limit as  $A \rightarrow \infty$ . Do you get the same answer as before?
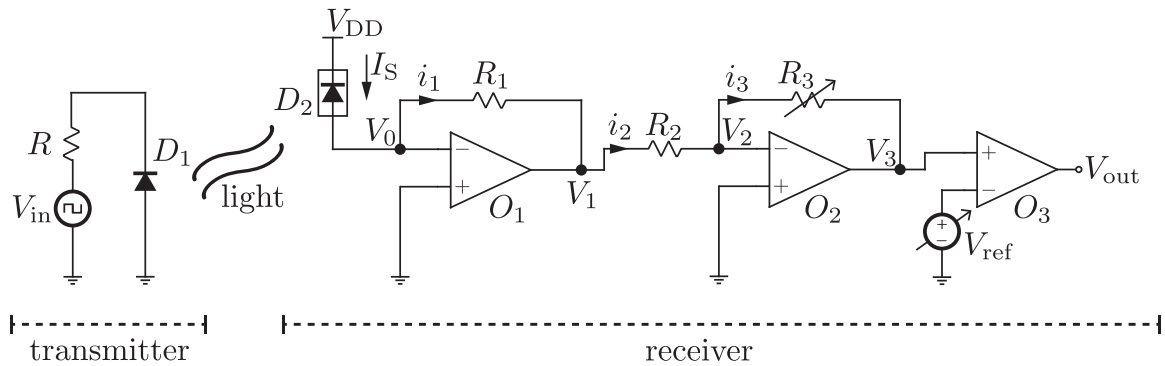
## 9. Wireless communication with an LED

**Note:** This problem is slightly more difficult (out of scope in difficulty) than a midterm problem. It was a HW problem from Fall 2015.

In this question, we are going to analyze the system shown in the figure below. It shows a circuit that can be used as a wireless communication system using visible light (or infrared, very similar to remote controls).





The element  $D_1$  in the transmitter is a light-emitting diode (LED in short). An LED is an element that emits light where the brightness of the light is controlled by the current flowing through it. You can recall controlling the light emitted by an LED using your MSP430 in touch screen lab part 1. In our circuit, the current across the LED, hence its brightness, can be controlled by choosing the applied voltage  $V_{in}$  and the value of the resistor  $R$ . In the receiver, the element labeled as  $D_2$  is a reverse biased solar cell. You can recall using a reverse biased solar cell in imaging labs 1 to 3 as a light controlled current source, by  $I_S$  we denote the current supplied by the solar cell. In this circuit the LED  $D_1$  is used as a means for transmitting information with light, and the reverse biased solar cell  $D_2$  is used as a receiver of light to see if anything was transmitted.

**Remark:** In imaging lab part 3, we have talked about how non-idealities such as background light affect the performance of a system that does light measurements. In this question we assume ideal conditions, that is, there is no source of light around except for the LED.

In our system, we define two states for the transmitter, the *transmitter is sending something* when they turn on the LED, and *transmitter is not sending anything* when they turn off the LED. On the receiver side, the goal is to convert the current  $I_S$  generated by the solar cell into a voltage and amplify it so that we can read the output voltage  $V_{out}$  to see if the transmitter was sending something or not. The circuit implements this operation through a series of op-amps. It might look look complicated at first glance, but we can analyze it a section at a time.

- Currents  $i_1$ ,  $i_2$  and  $i_3$  are labeled on the diagram. Assuming the Golden Rules hold, is  $I_S = i_1$ ?  $i_1 = i_2$ ?  $i_2 = i_3$ ? Treat the solar cell as an ideal current source.
- Use the Golden Rules to find  $V_0$ ,  $V_1$ ,  $V_2$  and  $V_3$  in terms of  $I_S$ ,  $R_1$ ,  $R_2$  and  $R_3$ .  
**Hint:** Solve for them from left to right, and remember to use the op-amp golden rules.
- In the previous part, how could you check your work to gain confidence that you got the right answer?
- Now, assume that the transmitter has chosen the values of  $V_{in}$  and  $R$  to control the intensity of light emitted by LED such that when *transmitter is sending something*  $I_S$  is equal to 0.1 A, and when the *transmitter is not sending anything*  $I_S$  is equal to 0 A. The following figure shows a visual example of how this current  $I_S$  might look like as time changes (note that this is just here for helping visualizing the form of the current supplied by the solar cell).



For the receiver, suppose  $V_{\text{ref}} = 2V$ ,  $R_1 = 10\Omega$ ,  $R_2 = 1000\Omega$ , and the supply voltages of the op-amps are  $V_{\text{DD}} = 5V$  and  $V_{\text{SS}} = -5V$ . Pick a value of  $R_3$  such that  $V_{\text{out}}$  is  $V_{\text{DD}}$  when the *transmitter is sending something* and  $V_{\text{SS}}$  when the *transmitter is not sending anything*?

(e) In the previous part, how could you check your work to gain confidence that you got the right answer?

## 10. Wine Barrel Filler

You own a wine tasting place in Berkeley! You have a very elegant dispenser set up for each kind of wine. To minimize the number of bottles you use, you dispense the wine directly from refillable rectangular barrels. To make sure that the barrels never run out, you want to design a level “detector” which will send the appropriate signal to the tank of wine to pour wine into a barrel until a certain level. Two lateral faces of the barrel (opposite to each other) are coated inside with a perfectly conducting material and you have wires coming out of the barrel at the two faces. You are given that the resistivity of wine is  $\rho$ . The dimensions of the barrels (other than height) are  $l$  and  $w$ . Design a circuit to control the level of the wine. You don’t want it to go below a threshold  $h_{\text{min}}$  and above a threshold  $h_{\text{max}}$ . The only commands the circuit needs to output are “Fill” and “Stop Fill”. Recall the formula  $R = \frac{\rho l}{A}$ .

